



LM339 dc-dc converter
 19/05/06 Eleken
 rev_c1815@yahoo.co.jp

Icc(quietent) = 14mA
 Vout(+) = 14.92V, Vout(-) = -14.89V

- Load Test
 Iout(+) = 15mA, Iout(-) = 0mA
 Icc = 68mA, Vout(+) = 14.92V

Iout(+) = 0mA, Iout(-) = -15mA
 Icc = 94mA, Vout(-) = -14.67V

Iout(+) = |Iout(-)| = 20mA
 Icc = 212mA, Vout(+) = 14.94V, Vout(-) = -14.43V

Iout(+) = |Iout(-)| = 27mA
 Icc = 259mA, Vout(+) = 14.94V, Vout(-) = -11.77V